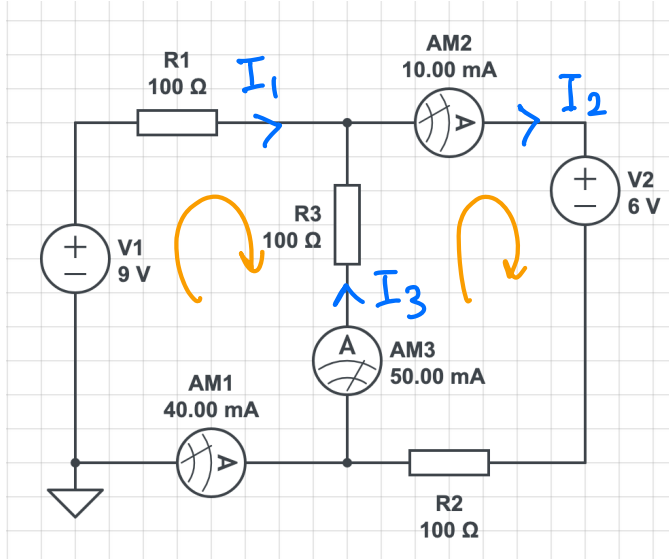


Write down a matrix-vector equation where the unknown is a vector of currents, I_1 , I_2 and I_3 . Verify that the ammeter values shown in this diagram are correct.



$$\begin{aligned} +9 - 100 I_1 + 100 I_3 &= 0 \\ -100 I_3 - 6 - 100 I_2 &= 0 \\ I_1 + I_3 &= I_2 \end{aligned}$$

$$\begin{bmatrix} -100 & 0 & +100 \\ 0 & -100 & -100 \\ 1 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -9 \\ 6 \\ 0 \end{bmatrix}$$

Solving the above with Doolittle's method Write down the system matrix, A , using Kirchhoff's Laws and find its LU Decomposition using Doolittle's method. What is the right-hand side?

$$\begin{bmatrix} A_{11} & A_{12} & A_{13} \\ A_{21} & A_{22} & A_{23} \\ A_{31} & A_{32} & A_{33} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \\ b_3 \end{bmatrix}$$

In the following decomposition, determine all the entries such as L_{21} and U_{12} .

$$A = \begin{bmatrix} 1 & 0 & 0 \\ L_{21} & 1 & 0 \\ L_{31} & L_{32} & 1 \end{bmatrix} \begin{bmatrix} U_{11} & U_{12} & U_{13} \\ 0 & U_{22} & U_{23} \\ 0 & 0 & U_{33} \end{bmatrix}$$

Use L and U to calculate the value of the currents in the circuit.

For Doolittle's method, use Gaussian Elimination

$$\begin{bmatrix} -100 & 0 & +100 \\ 0 & -100 & -100 \\ 1 & -1 & 1 \end{bmatrix}$$

$$\text{row 2} = \text{row 2} - 0 \times \text{row 1}$$

$$\text{row 3} = \text{row 3} - \left(-\frac{1}{100}\right) \times \text{row 1}$$

$$1 - \frac{-1}{100} \times -100 \rightarrow 0, \quad -1 - (\dots) \times 0, \quad 1 - \left(-\frac{1}{100}\right) \times 100$$

$$0, \quad -1, \quad 2$$

Now matrix is

$$\begin{bmatrix} -100 & 0 & +100 \\ 0 & -100 & -100 \\ 0 & -1 & 2 \end{bmatrix}$$

$$\text{row 3} = \text{row 3} - \frac{1}{100} \times \text{row 2}$$

$$0 - \frac{1}{100} \times 0, \quad -1 - \frac{1}{100} \times -100 \rightarrow 0, \quad 2 - \frac{1}{100} \times -100$$

$$0, \quad 0, \quad 2+1$$

$$\begin{bmatrix} -100 & 0 & 100 \\ 0 & -100 & -100 \\ 0 & 0 & 3 \end{bmatrix} = U. \quad L = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -\frac{1}{100} & \frac{1}{100} & 1 \end{bmatrix}$$

$$L \underbrace{U}_Y x = b \quad \text{or} \quad A x = b$$

$Ly = b$ by forward elimination.

$$b = \begin{bmatrix} -9 \\ 6 \\ 0 \end{bmatrix} \quad \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -\frac{1}{100} & \frac{1}{100} & 1 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \\ y_3 \end{bmatrix} = \begin{bmatrix} -9 \\ 6 \\ 0 \end{bmatrix}$$

$$y_1 = -9$$

$$0x - 9 + y_2 = 6 \Rightarrow y_2 = 6$$

$$+\frac{9}{100} + \frac{6}{100} + y_3 = 0 \Rightarrow y_3 = -\frac{15}{100} = -\frac{3}{20}$$

Now, $Ux = y$ by backward elimination

$$\begin{bmatrix} -100 & 0 & 100 \\ 0 & -100 & -100 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} -9 \\ 6 \\ -0.15 \end{bmatrix}$$

$$1) \quad 3x_3 = -0.15 \Rightarrow \boxed{x_3 = -0.05}$$

$$2) \quad \begin{aligned} -100x_2 - 100x_3 &= 6 \\ -100x_2 + 5 &= 6 \end{aligned} \Rightarrow \boxed{x_2 = -0.01}$$

$$3) \quad \begin{aligned} -100x_1 + 100x_3 &= -9 \\ -100x_1 - 5 &= -9 \end{aligned} \Rightarrow \boxed{x_1 = 0.04}$$

$$I_1 = 40 \text{ mA}$$

$$I_2 = -10 \text{ mA}$$

$$I_3 = -5 \text{ mA}$$

Calculate the currents when (a) $V_1 = 5$ and $V_2 = 4$ Volts, and (b) $V_1 = 100$ and $V_2 = 1$ Volts. Use the LU decomposition each time.

The same LU decomposition can be used: $b_1 = -V_1$
 $b_2 = +V_2$

$$\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ -\frac{1}{100} & \frac{1}{100} & 1 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \\ y_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 4 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{aligned} y_1 &= -5 \\ y_2 &= 4 \\ y_3 &= ? \end{aligned} \quad \begin{aligned} -\frac{5}{100} + \frac{4}{100} + y_3 &= 0 \\ \Rightarrow y_3 &= -0.09 \end{aligned}$$

$$\begin{bmatrix} -100 & 0 & 100 \\ 0 & -100 & -100 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} -5 \\ 4 \\ -\frac{9}{100} \end{bmatrix} \Rightarrow \begin{aligned} x_3 &= -0.03 \\ x_2 &= -0.01 \\ x_1 &= +0.02 \end{aligned}$$

$$\begin{aligned} -100x_2 - 100x \frac{-3}{100} &= 4, & -100x_2 &= 4-3 \\ -100x_1 + 100x \frac{-3}{100} &= -5, & -100x_1 &= -5+3 \end{aligned}$$